

Lecture 07

DC and AC Load Line


- DC biasing circuits
- DC and AC equivalent circuit
- Q-point (Static operation point)
- DC and AC load line
- Saturation Cutoff Condition
- Compliance

Book Reference

- Electronic Devices and Circuit Theory by Robert Boylestad & Louis Nashelsky
(Prentice Hall)
- Electronic Devices by Thomas L. Floyd
(Prentice Hall)

DC Biasing Circuits

 - The **ac** operation of an amplifier depends on the initial **dc** values of I_B , I_C , and V_{CE} .
- By varying I_B around an initial dc value, I_C and V_{CE} are made to vary around their initial dc values.
- **DC** biasing is a static operation since it deals with setting a **fixed (steady)** level of current (through the device) with a desired fixed voltage drop across the device.




Purpose of the DC biasing circuit

- To turn the device “ON”
- To place it in operation in the region of its characteristic where the device operates most linearly, i.e. to set up the initial dc values of I_B , I_C , and V_{CE}


Voltage-Divider Bias

- The voltage – divider (or potentiometer) bias circuit is by far the most commonly used.
- R_{B1}, R_{B2}
 \Rightarrow voltage-divider to set the value of V_B, I_B
- C_3
 \Rightarrow to **short circuit ac** signals to ground, while not effect the DC operating (or biasing) of a circuit
($R_E \Rightarrow$ stabilizes the ac signals)

\rightarrow **Bypass Capacitor**

 

Graphical DC Bias Analysis

 


$$V_{CC} - I_C R_C - V_{CE} - I_E R_E = 0$$

$$\text{for } I_C \approx I_E$$

$$I_C = \frac{-1}{R_C + R_E} V_{CE} + \frac{V_{CC}}{R_C + R_E}$$

Point - slope form of straight line equation :



$$y = mx + c$$

 

DC Load Line

- The straight line is known as the **DC load line**
- Its significance is that regardless of the behavior of the transistor, the collector current I_C and the collector-emitter voltage V_{CE} must always lie on the load line, depends **ONLY** on the V_{CC} , R_C and R_E
- (i.e. The dc load line is a graph that **represents all the possible combinations of I_C and V_{CE} for a given amplifier**. For every possible value of I_C , and amplifier will have a corresponding value of V_{CE} .)
- It must be true at the same time as the transistor characteristic. Solve two conditions using simultaneous equations

→ graphically → **Q-point !!**

  


What is $I_{C(sat)}$ and $V_{CE(off)}$?

Q-Point (Static Operation Point)

- When a transistor does not have an **ac input**, it will have **specific dc values** of I_C and V_{CE} .
- These values correspond to a specific point on the **dc load line**. This point is called the ***Q-point***.
- The letter ***Q*** corresponds to the word (Latent) **quiescent**, meaning **at rest**.
- A quiescent amplifier is one that has no ac signal applied and therefore has constant dc values of I_C and V_{CE} .


Q-Point (Static Operation Point)

 - The intersection of the dc bias value of I_B with the dc load line determines the Q -point.
- It is desirable to have the Q -point centered on the load line. Why?
- When a circuit is designed to have a centered Q -point, the amplifier is said to be midpoint biased.
- Midpoint biasing allows optimum ac operation of the amplifier.




DC Biasing + AC signal


- When an **ac signal** is applied to the base of the transistor, I_C and V_{CE} will both vary around their Q -point values.
- When the Q -point is **centered**, I_C and V_{CE} can both make the **maximum** possible transitions above and below their initial dc values.
- When the Q -point is **above** the center on the load line, the input signal may cause the transistor to saturate. When this happens, a part of the output signal will be **clipped** off.
- When the Q -point is **below** midpoint on the load line, the input signal may cause the transistor to cutoff. This can also cause a portion of the output signal to be clipped.

 


DC Biasing + AC signal

 

(a) Limited by saturation

 


(b) Limited by cutoff

 


(c) Centered Q-point


DC and AC Equivalent Circuits

 

Bias Circuit

 


DC equivalent circuit


 


AC equivalent circuit

AC Load Line

 

  - The ac load line of a given amplifier will **not follow** the plot of the dc load line.
- This is due to the dc load of an amplifier is different from the ac load.




AC Load Line

What does the ac load line tell you?

- The ac load line is used to tell you the maximum possible output voltage swing for a given common-emitter amplifier.
- In other words, the ac load line will tell you the maximum possible peak-to-peak output voltage (V_{pp}) from a given amplifier.
- This maximum V_{pp} is referred to as the **compliance** of the amplifier.

(AC Saturation Current $I_{c(sat)}$, AC Cutoff Voltage $V_{CE(off)}$)


 
AC Saturation Current and AC Cutoff Voltage



Amplifier Compliance

- The ac load line is used to tell the *maximum possible output voltage swing for a given common-emitter amplifier*. In another words, the ac load line will tell the maximum possible peak-to-peak output voltage (V_{PP}) from a given amplifier. This maximum V_{PP} is referred to as the *compliance* of the amplifier.
- The compliance of an amplifier is found by determine the maximum possible of I_C and V_{CE} from their respective values of I_{CQ} and V_{CEQ} .

Maximum Possible Compliance

  

Compliance

The maximum possible transition for V_{CE} is equal to the difference between $V_{CE(off)}$ and V_{CEQ} . Since this transition is equal to $I_{CQ}r_C$, the maximum peak output voltage from the amplifier is equal to $I_{CQ}r_C$. Two times this value will give the maximum peak-to-peak transition of the output voltage:

$$\boxed{V_{PP} = 2I_{CQ}r_C} \quad \text{—————} \quad (A)$$

V_{PP} = the output compliance, in peak-to-peak voltage

I_{CQ} = the quiescent value of I_C

r_C = the ac load resistance in the circuit

Compliance


When $I_C = I_{C(sat)}$, V_{CE} is ideally equal to 0V. When $I_C = I_{CQ}$, V_{CE} is at V_{CEQ} . Note that when I_C makes its maximum possible transition (from I_{CQ} to $I_{C(sat)}$), the output voltage changes by an amount equal to V_{CEQ} . Thus the maximum peak-to-peak transition would be equal to twice this value:

$$\boxed{V_{PP} = 2V_{CEQ}} \quad \text{—————} \quad \text{(B)}$$

- Equation (A) sets the limit in terms of $V_{CE(off)}$. If the value obtained by this equation is exceeded, the output voltage will try to exceed $V_{CE(off)}$, which is not possible. This is called cutoff clipping, because the output voltage is clipped off at the value of $V_{CE(off)}$.
- Equation (B) sets of the limit in terms of $I_{C(sat)}$. If the value obtained by this equation is exceeded, the output will experience saturation clipping.

Cutoff and Saturation Clipping

 - When determining the output compliance for a given amplifier, solve both equation (A) and (B). *The lower of the two results is the compliance of the amplifier.*



Example

- For the voltage-divider bias amplifier shown in the figure, what is the ac and dc load line. Determine the maximum output compliance.

