
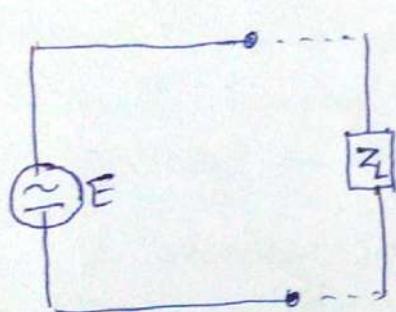

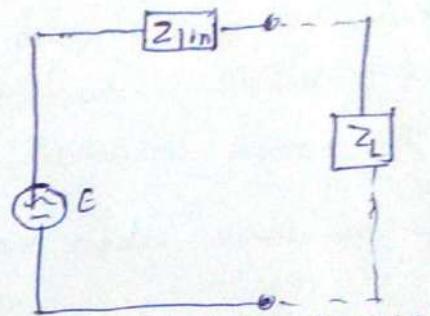
## Network Analysis and Network Theorems

Any electrical circuit containing resistors, capacitances, inductances and generators (i.e. source) is known as electrical network. The circuit elements are of two types a) passive and b) active. The inductor, resistor and capacitor with two terminals are regarded as passive elements as they are not fundamental source of power. The active elements are those which feed the power in to the given circuits. There are of two types a) voltage source and b) current source.



a) Ideal Voltage Generator  
(a)




b) Real voltage Source


An ideal voltage source is an active device which can maintain a constant voltage across its terminals irrespective of the current supplied by it. It is also called constant voltage source. It is always equal to the open circuit voltage (above circuit).

A real voltage source has a finite internal impedance therefore the potential difference across its terminals decreases with increase of load impedance (fig(b))

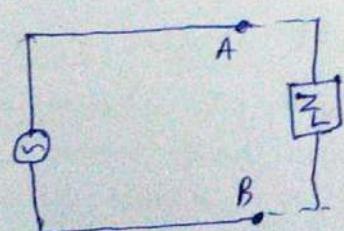A constant current source is an active device which can supply the constant current to any load resistance that is connected across its terminals.



a) Ideal current Source

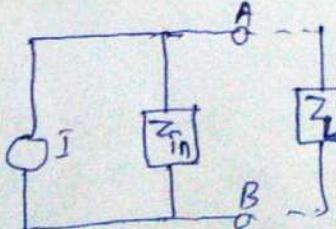

b) Real current Source


A Real source is a power source which contains a finite internal parallel impedance (fig. b)

### Networks - some Important Definitions

From the network

Junction (Node).1 -

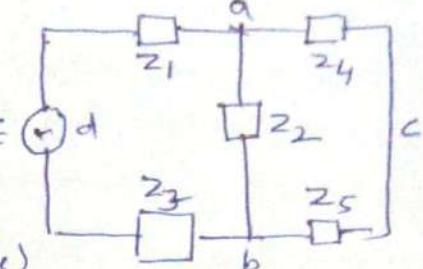The point where two or more branches meet is called a junction (or node)  
a and b are junctions



Branch 1 In a network any group of series elements having two terminals is called a branch.  
The current in a branch remains same at each point.

An element joining two nodes, such as a and b, in fig. is called a branch.

A set of branches forming a closed path in a network is called mesh.

Loop! - Any closed path in a network is called a loop.  
acba and abda are loops.

Active and passive Networks! - The networks containing sources of emf are called active networks, networks containing no sources of emf are called passive networks


Linear and Non-linear Networks! - The network is said to be a linear, if it consists of linear impedances. A linear impedance is any impedance that obeys ohm's law. In non-linear networks, the relation voltage and current will be non-linear

### Net work Theorem

Statement! - In any linear network containing impedances and more than one source of emf, the current flowing in any element is equal to algebraic sum of the currents that will separately flow in that element if each source

of emf, were considered separately all the other sources being replaced at that time by their internal impedances.

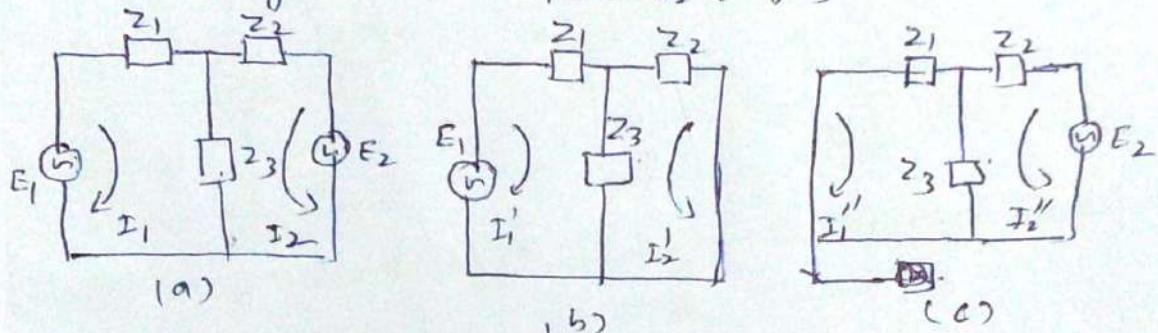Proof! - Let us consider the network with two sources of emf's  $E_1$  and  $E_2$  with internal impedances  $z_1$  and  $z_2$  respectively, (fig) let the current due to  $E_1$  and  $E_2$  acting together be  $I_1$  and  $I_2$  (fig a), let current due to emf  $E_1$  acting alone be  $I'_1$  and  $I'_2$  (fig b) let the current due to  $E_2$  acting alone be  $I''_1$  and  $I''_2$  (fig c)



Applying Kirchhoff's II law to fig(a) the mesh equations are

$$E_1 = (z_1 + z_3) I_1 + z_3 I_2 \quad \text{--- (1)}$$

$$E_2 = z_3 I_1 + (z_2 + z_3) I_2 \quad \text{--- (2)}$$

when  $E_1$  is considered to act alone fig(b) the mesh equations are

$$E_1 = (z_1 + z_3) I'_1 + z_3 I'_2 \quad \text{--- (3)}$$

$$0 = z_3 I'_1 + (z_2 + z_3) I'_2 \quad \text{--- (4)}$$

when  $E_2$  is considered to act alone fig(c) the mesh equations are

$$0 = (z_1 + z_3) I''_1 + z_3 I''_2 \quad \text{--- (5)}$$

$$E_2 = z_3 I''_1 + (z_2 + z_3) I''_2 \quad \text{--- (6)}$$

Adding eqn (3) and (5)  $E_1 = (z_1 + z_3)(I'_1 + I''_1) + z_3(I'_2 + I''_2)$

Adding eqn (4) & (6)

$$E_2 = (z_2 + z_3)(I'_2 + I''_2) + z_3(I'_1 + I''_1) \quad \text{--- (7)}$$

Eqn (7) and (8) will be identical with Eqn (1) and (2) if

$$I_1 = I'_1 + I''_1 \quad \text{and} \quad I_2 = I'_2 + I''_2$$



Thus the theorem proved.

(3)
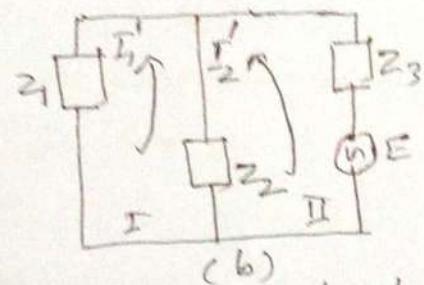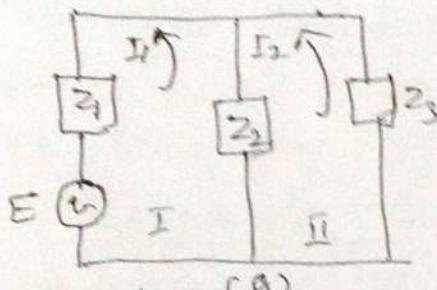
## Reciprocity Theorem

Statement: If an emf applied in one mesh of network of linear impedances produces a certain current in the second mesh, then the same emf acting in the second mesh will give an identical current in the first mesh.

Proof: Consider a network [fig(a)] Here the source of emf  $E$  is in the first mesh. Let the currents in the first and second meshes be  $I_1$  and  $I_2$  respectively,



Applying Kirchhoff's II Law to the two meshes

$$I_1(Z_1 + Z_2) - I_2 Z_2 = E \quad \text{--- (1)}$$

and  $I_2(Z_2 + Z_3) - I_1 Z_2 = 0 \quad \text{--- (2)}$

Substituting the value of  $I_1$  from eqn (2) in eqn (1) we get

$$I_2 \left[ \frac{(Z_1 + Z_2)(Z_2 + Z_3)}{Z_2} - Z_2 \right] = E$$

$$\text{or } I_2 = \frac{E \cdot Z_2}{(Z_1 + Z_2)(Z_2 + Z_3) - Z_2^2} \quad \text{--- (3)}$$

Consider the network b) [fig(b)]. Here the source of emf is in the second mesh, let the current in the first and second meshes be  $I_1'$  &  $I_2'$  respectively.

Applying Kirchhoff's II Law to the two meshes we get

$$I_1'(Z_1 + Z_2) - I_2' Z_2 = 0 \quad \text{--- (4)}$$

$$\& I_2'(Z_2 + Z_3) - I_1' Z_2 = E \quad \text{--- (5)}$$

Substituting the value of  $I_2'$  from eqn (4) in eqn (5) we get

(4)

$$I_1' \left[ \frac{(Z_1 + Z_2)(Z_2 + Z_3)}{Z_2} - Z_2 \right] = E$$

$$\text{or } I_1' = \frac{E \cdot Z_2}{(Z_1 + Z_2)(Z_2 + Z_3) - Z_2^2} \quad \text{--- (4)}$$

Comparing Eqn (3) and Eqn (4) we have

$$I_2 = I_1'$$



Thus the reciprocity theorem is proved.

Transfer Impedance! - The ratio of emf  $E$  in one mesh to the current  $I$  in another mesh is called the transfer Impedance  $Z_T$ .
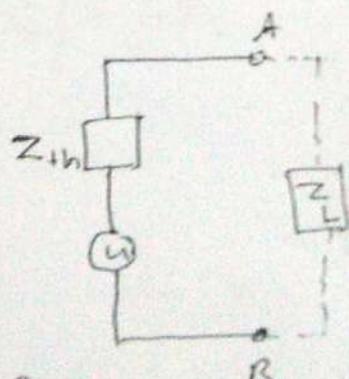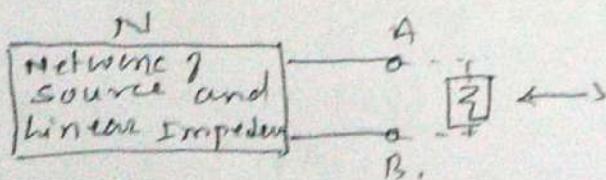
### Thevenin's Theorem

Statement! - The current in a load impedance connected between two terminals of a network of sources and linear impedances is same as due to a single voltage source of emf equal to open circuit voltage between the same terminals of the network and internal impedance equal to the impedance of the network between the same terminals of the network, when all the sources in the network have been replaced by their internal impedances.

The schematic representation of Thevenin's theorem as shown in fig.




$N$  is a network containing a number of sources and linear impedances with output terminals  $A$  and  $B$ . Let  $E_{th}$  be the open-circuit voltage

across A and B. Let  $Z_{th}$  be the impedance measured between two terminals A and B, when all the sources have been replaced by their respective internal impedance. The network N will produce the same current in an external load impedance  $Z_L$  connected across A and B, as a single voltage source of emf  $E_{th}$  and internal impedance  $Z_{th}$  would do.

Proof: consider a network containing resistive impedance  $Z_1$ ,  $Z_2$  and  $Z_3$  and one source of emf  $E$  and internal impedance zero (i.e. ideal source) (fig(i))

$I_1$  is the current supplied by the source,  $I_2$  is the current flowing through the load impedance  $Z_L$

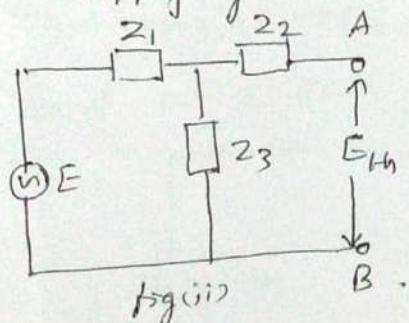Applying Kirchhoff's law to the mesh I and II we get



$$I_1 Z_1 + (I_1 - I_2) Z_3 = E \quad (1)$$

$$\text{or } I_1 (Z_1 + Z_3) - I_2 Z_3 = E \quad (1)$$

$$\text{and } I_2 Z_2 + I_2 Z_L - (I_1 - I_2) Z_3 = 0.$$

$$I_2 (Z_2 + Z_L + Z_3) = I_1 Z_3 \quad (2)$$

$$\text{or } I_1 = \frac{I_2 (Z_2 + Z_3 + Z_L)}{Z_3}$$

Substituting the value of  $I_1$  in eqn(1) we get

$$I_2 \frac{(Z_2 + Z_3 + Z_L)}{Z_3} (Z_1 + Z_2) - I_2 Z_3 = E$$

$$\text{or } I_2 [(Z_2 + Z_3 + Z_L)(Z_1 + Z_2) - Z_3^2] = EZ_3$$

$$\text{or } I_2 = \frac{EZ_3}{Z_2(Z_1 + Z_3) + Z_1 Z_3 + Z_L(Z_1 + Z_3)}$$


$$\therefore I_2 = \frac{EZ_3 / (Z_1 + Z_3)}{Z_1 + \left( \frac{Z_1 Z_3}{Z_1 + Z_3} \right) + Z_L} \quad (3)$$

Again from the fig(i) the open circuit voltage across terminals A & B. (i.e. when  $Z_L$  is removed) is

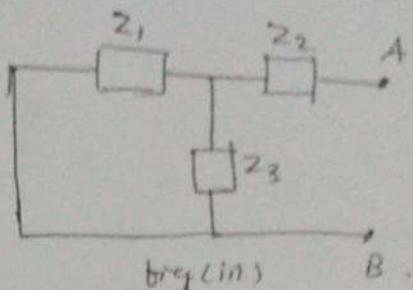(6)

$$E_{th} = \frac{E^2 z_3}{z_1 + z_3} \quad \text{--- (4)}$$

Further if  $E$  is replaced by  
by zero internal impedance  
by  $(i)$  the impedance of network  
between  $A$  and  $B$  is




$$Z_{th} = z_2 + \frac{\frac{1}{z_1} + \frac{1}{z_3}}{\frac{1}{z_1} + \frac{1}{z_3}}$$

$$= z_2 + \frac{z_1 z_3}{z_1 + z_3} \quad \text{--- (5)}$$

Thus Eqn (3) is equivalently written as.

$$I_2 = \frac{E_{th}}{Z_{th} + Z_L} \quad \text{--- (6)}$$

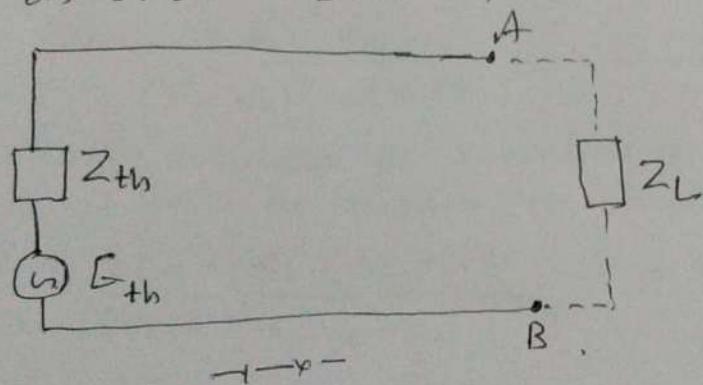This proves Thévenin's theorem. The equivalent circuit as shown below.




### Maximum power Transfer theorem

- Statement :- The maximum power will be delivered  
to a load by a source when
- i) resistive component of the impedance of load and source  
are equal and.
  - ii) The reactive components of the impedances of source  
and load are equal in magnitude but opposite in sign
- Proof - consider a voltage source of emf  $E'$  and  
complex internal impedance  $z'$  and a load of,

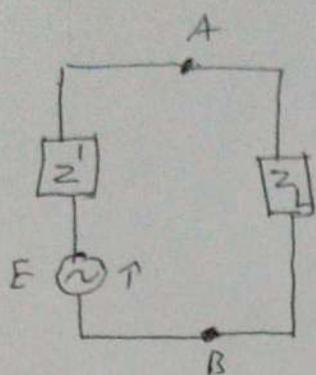(7)

Complex impedance  $Z_L$  connected across the source



Now we have

$$Z = R' + jX' \quad \text{--- (1)}$$

$$\text{and } Z_L = R_L + jX_L \quad \text{--- (2)}$$

Here  $R'$  and  $R_L$  are the resistive components and  $X'$  and  $X_L$  are the reactive components of  $Z$  &  $Z_L$  respectively.

The current  $I$  flowing in the circuit is

$$I = \frac{E'}{Z' + Z_L}$$

$$\text{or } I = \frac{E'}{(R' + R_L) + j(X' + X_L)} \quad \text{--- (3)}$$

The power delivered to the load is

$$P = I^2 R_L$$

$$\text{or } P = \frac{(E')^2 R_L}{(R' + R_L)^2 + (X' + X_L)^2} \quad \text{--- (4)}$$

Now let us consider the variation of  $P$  with  $X_L$ . The power  $P$  will be maximum when  $(\partial P / \partial X_L) = 0$ .

$$\frac{\partial P}{\partial X_L} = \frac{2(E')^2 R_L (X_L + X')}{[(R_L + R')^2 + (X_L + X')^2]^2} = 0.$$

$$\text{or } X_L = -X' \quad \text{--- (5)}$$

Thus if  $X'$  is inductive the  $X_L$  must be capacitive and of same magnitude of  $X'$ . When this condition is satisfied, the maximum power is

$$P_{max} = \frac{(E')^2 R_L}{(R_L + R')^2} \quad \text{--- (6)}$$

Again consider the variation of  $P_{max}$  with  $R_L$ . The power  $P_{max}$  with  $R_L$ . The power  $P_{max}$  will be maximum when

$$\frac{\partial P_{max}}{\partial R_L} = \frac{(E')^2 (R_L + R')^2 - 2(E')^2 R_L (R_L + R')}{(R_L + R')^4} = 0,$$

$\therefore R_L = R' \quad \text{--- (7)}$  Shows that maximum power will be delivered to the load when the resistive components of source and load are equal. The expression for the max. power may be written from Eqn (6)  $P_{max} = \frac{E'^2 R_L}{(2R_L)^2} = \frac{(E')^2}{4R_L} \quad \text{--- (8)}$